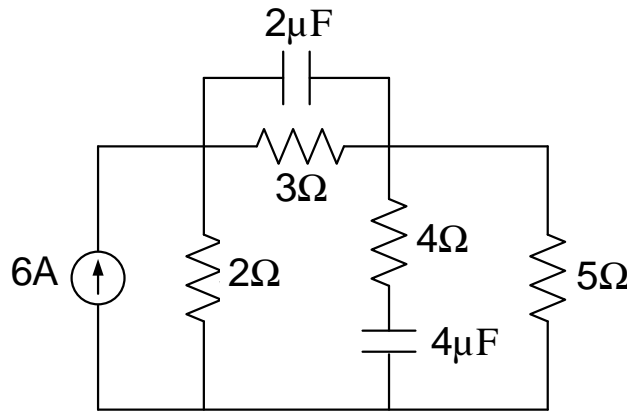


Basic Electrical Engineering Tutorial sheet 3 (Transients)

Q1: Find the energy (E_1 and E_2) stored in the 2 capacitors (2 and $4\mu\text{F}$) at steady state.


$$[E_1 = 12.96\mu\text{J} \text{ and } E_2 = 72\mu\text{J}]$$




Q2 A $50\mu\text{F}$ capacitor and a 20000Ω resistor are connected in series across a battery of 100V at instant $t = 0$. At instant $t = 0.5\text{ sec}$, the voltage is suddenly increased to 150V . Find the charge on the capacitor at $t = 0.75\text{ sec}$.
 $[3.19 \times 10^{-3}\text{ C}]$

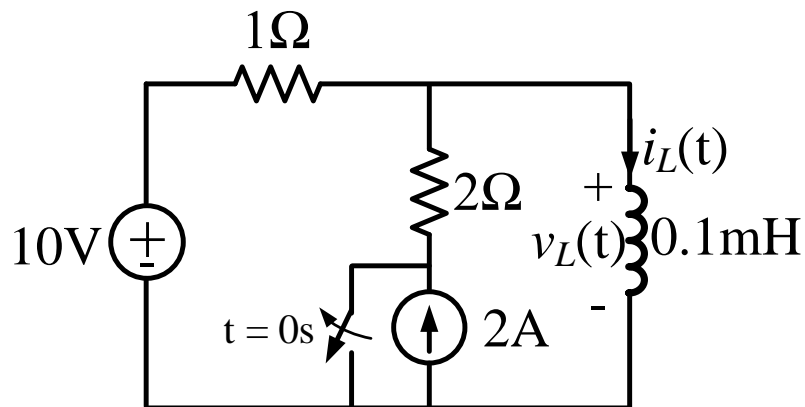Q3 Find the value of $i_L(t)$ and $v_L(t)$ at $t = 0.2\text{ms}$.

$$[i_L(0.2 \times 10^{-3}) = 11.73\text{ A and } v_L(0.2 \times 10^{-3}) = 0.27\text{ V.}]$$




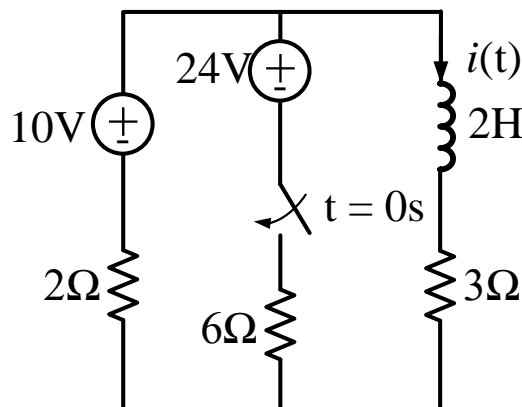Q4. Find the expression of current $i(t)$ for $t > 0\text{s}$ if the switch is closed at $t = 0\text{s}$. $[i(t) = 3 - e^{-\frac{9}{4}t}\text{ A}]$



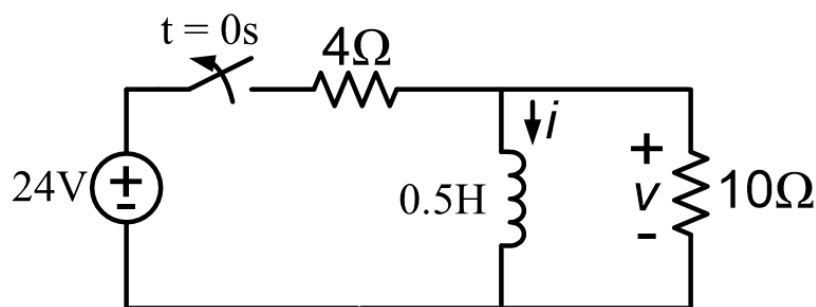
Q5 Find the value of voltage (v) across 10Ω resistor at $t = 5\text{ms}$ if the switch is open at $t = 0\text{s}$.

$$[v(5 \times 10^{-3}\text{s}) = -54.29\text{ V.}]$$




Q6 In the circuit, switch 1 is closed at $t = 0\text{s}$, and switch 2 is closed at 5s later. Find the value of inductor current $i(t)$ at $t = 10\text{s}$.

$$[i(10) = 4.09\text{ A}]$$

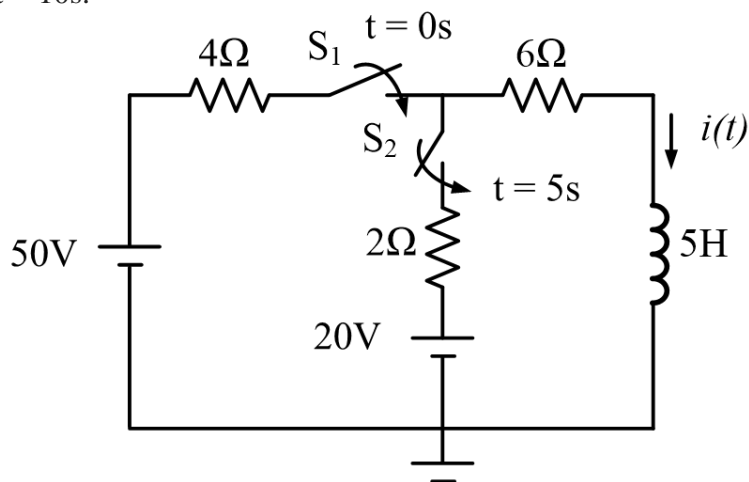


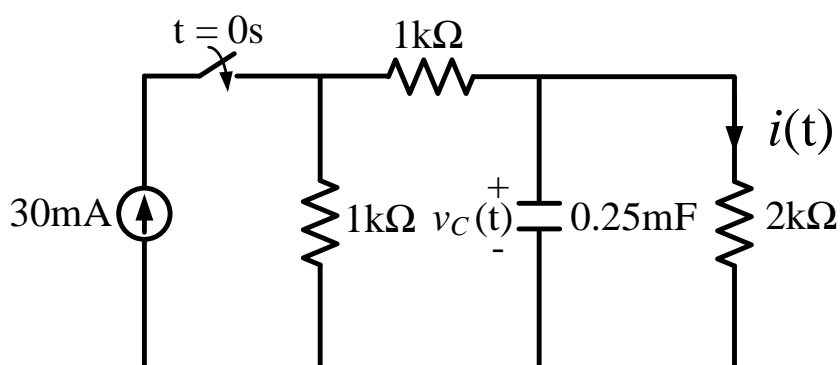Q7 Find the expression of voltage across capacitor ($v_C(t)$) and current ($i(t)$) through $2\text{k}\Omega$ resistor for $t > 0\text{s}$ if the switch is closed at $t = 0\text{s}$. [$v_C(t) = 15 - 15e^{-4t}\text{ V}$ and $i(t) = 7.5 - 7.5e^{-4t}\text{ mA}$.]




Q8 The switch in the circuit has been in position *a* for a long time. At $t = 0$ s, it moves to position *b*. Find the expression of $i(t)$ for $t > 0$ s.

$$[i(t) = -6e^{-0.25t} A]$$

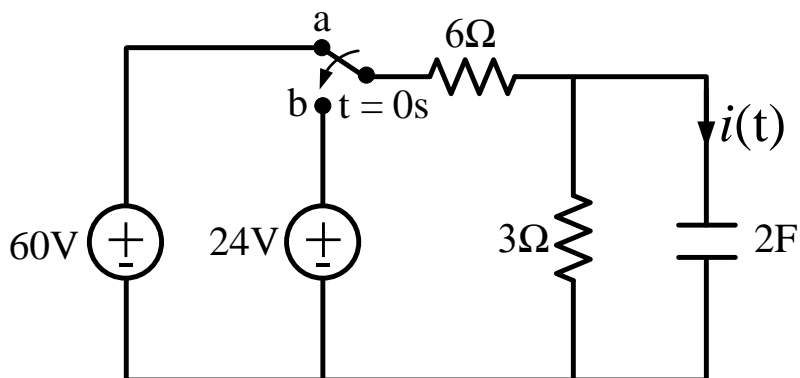

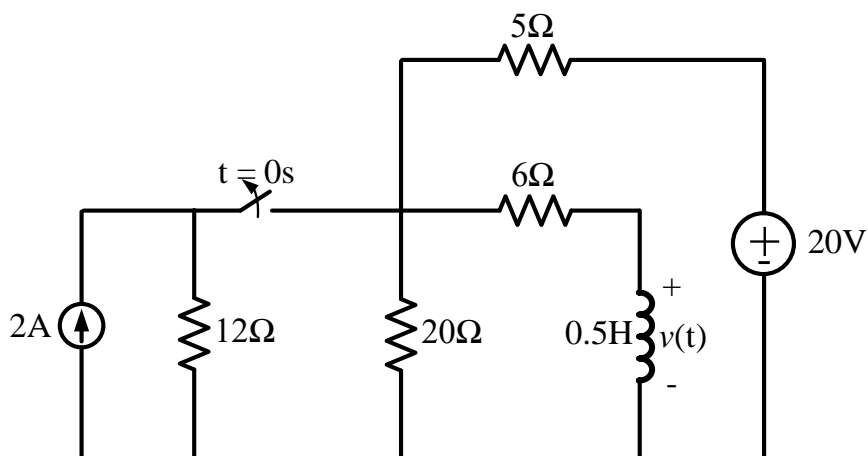Q9 Find the expression of voltage $v(t)$ for $t > 0$ s if the switch is open at $t = 0$ s. $[v(t) = -4e^{-20t} V]$




Q10. Find the values of (a) $i_L(0^+)$, $V_C(0^+)$, $V_R(0^+)$, $V_L(0^+)$

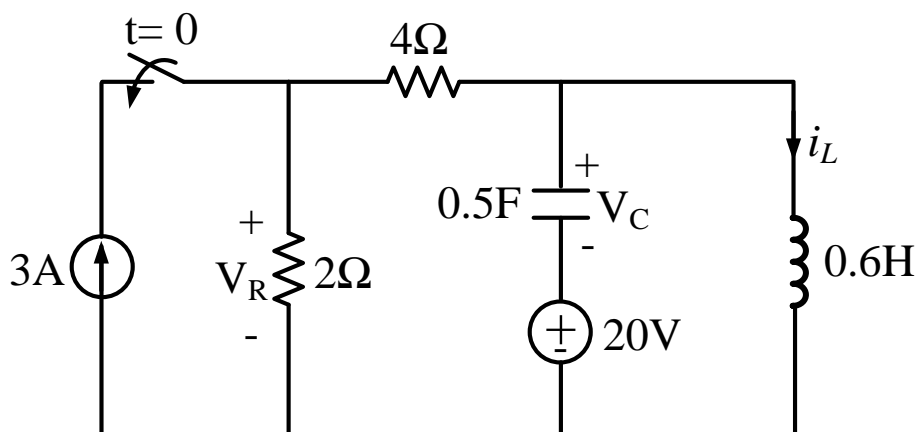(b) $i_L(\infty)$, $V_C(\infty)$, and $V_R(\infty)$ for the circuit shown.


$$[V_R(0^+) = 4V, V_C(0^+) = -20V, i_L(0^+) = 0A, V_L(0^+) = 0V]$$

$$[V_R(\infty) = 4V, V_C(\infty) = -20V \text{ and } i_L(\infty) = 1A]$$



Q11.

Find $i(t)$ and $v(t)$ in the circuit.

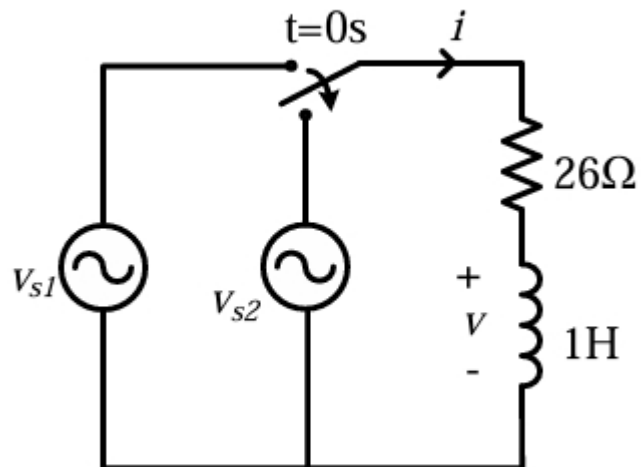

Where $v_{s1}=6\cos 15t$ and $v_{s2}=12\cos 15t$,

Ans: $i(t)=0.4\cos(15t-30^\circ)-0.173e^{-26t}$ A, $v(t)=6\cos(15t+60^\circ)+4.5e^{-26t}$ V