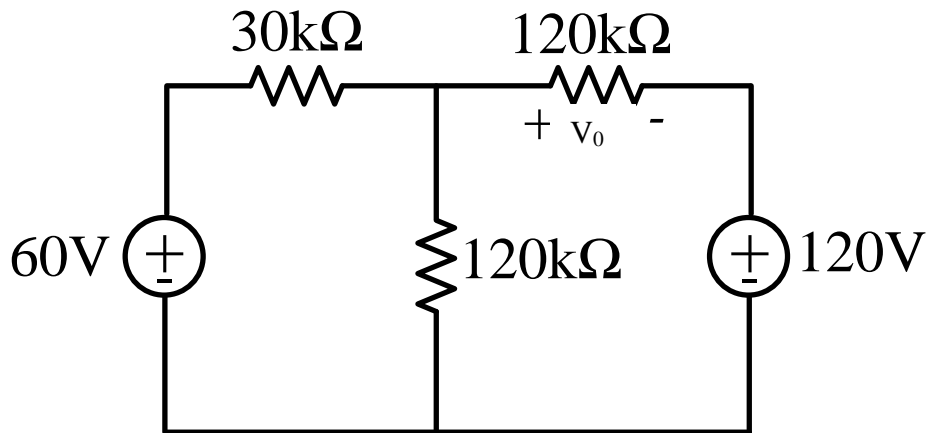



Tutorial-1

Q1 Obtain V_0 in the circuit using nodal voltage and loop current methods.

[Ans $V_0 = -60\text{V}$]




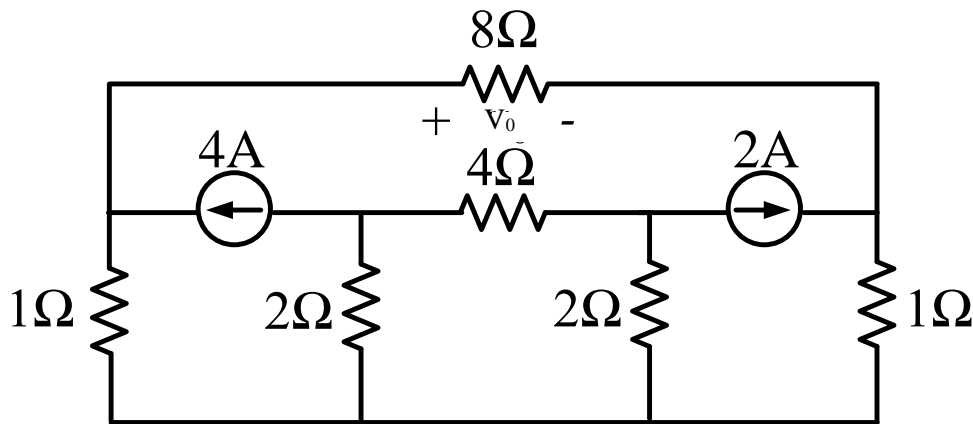Q2 Find V_0 in the circuit across the 8Ω resistor.




[Ans $V_0 = 1.6\text{ V}$]

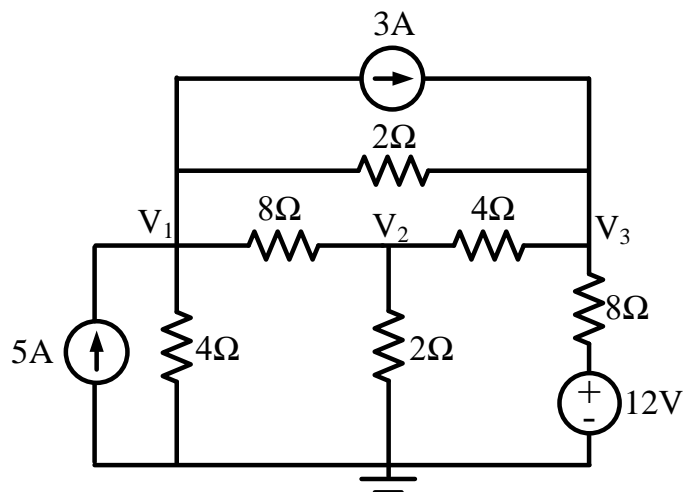Q 3: Find V_1 , V_2 , and V_3 in the circuit. [Ans $V_1 = 10\text{ V}$, $V_2 = 4.933\text{ V}$, and $V_3 = 12.267\text{ V}$]




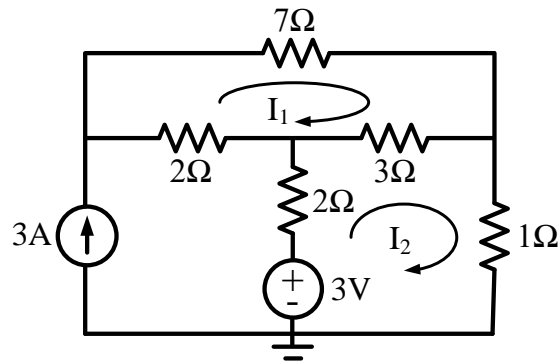Q4 Find the loop currents I_1 and I_2 in the circuit using mesh current method.




[Ans $I_1 = 1$ A and $I_2 = 2$ A]

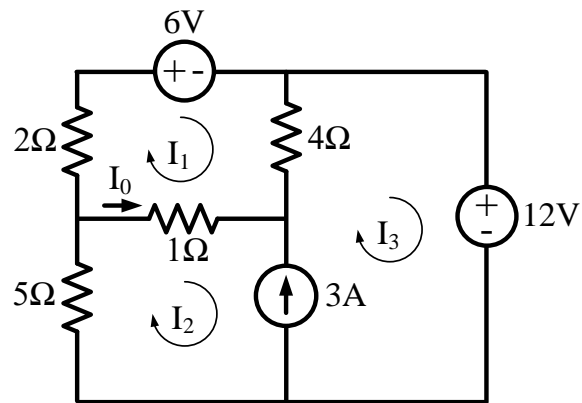Q5 Find I_0 in the circuit using mesh current method.




[Ans $I_0 = -1.733$ A]

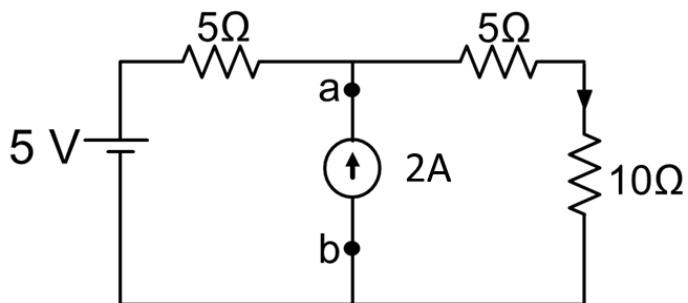Q6 Find the voltage (V_{ab}) across 2 A source using Thevenin's theorem.




[Ans $V_{ab} = 11.25$ V]

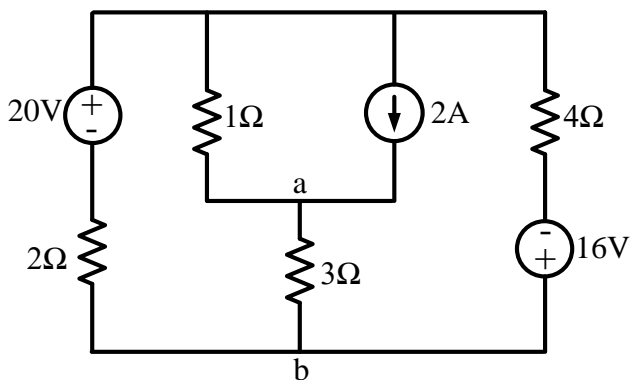Q7 Find the Norton equivalent across terminals ab and then find the voltage across 3Ω resistor in the circuit.




[Ans $R_N = (7/3) \Omega$, $I_N = (30/7) \text{ A}$, $V_{3\Omega} = (45/8) \text{ V}$]

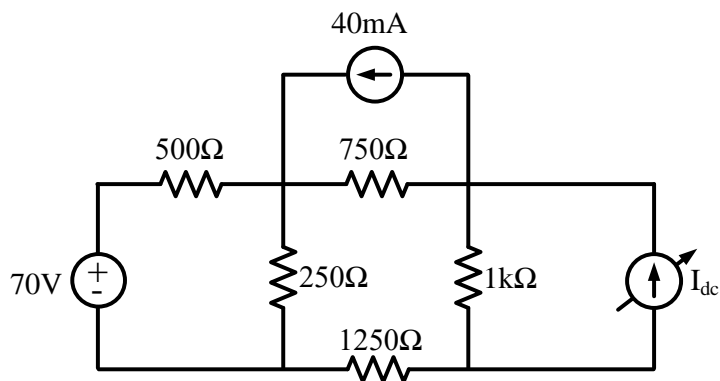Q8: Obtain the required value of the variable current source I_{dc} shown in the figure for which the power delivered by the 40mA current source will be zero.




[Ans $I_{dc} = 120\text{mA}$]

Q9 Find the maximum power that the active network to the left of terminals ab can deliver to the adjustable load resistor R_L .

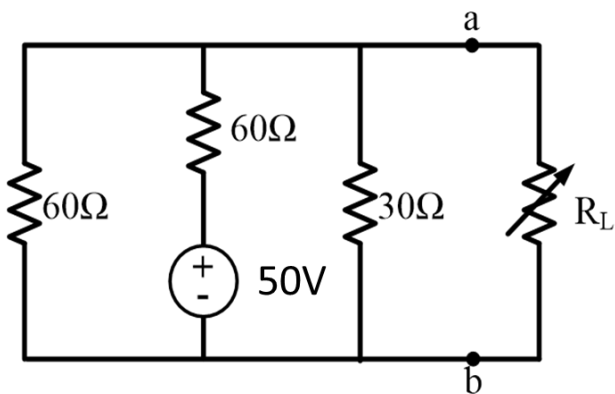


[Ans 2.60 W]

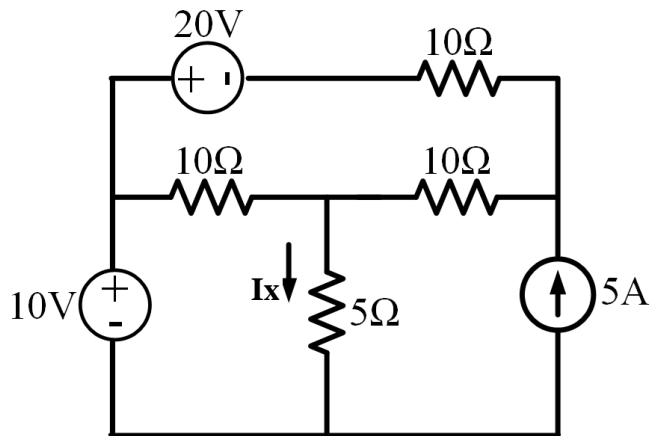Q10: While solving the circuit using superposition theorem, find the current (I_x) through 5Ω resistor contributed by 10V, 20V, and 5A sources individually. Ans [$\frac{1000}{1167}A$, $-\frac{4}{7}A$, $\frac{10}{7}A$]




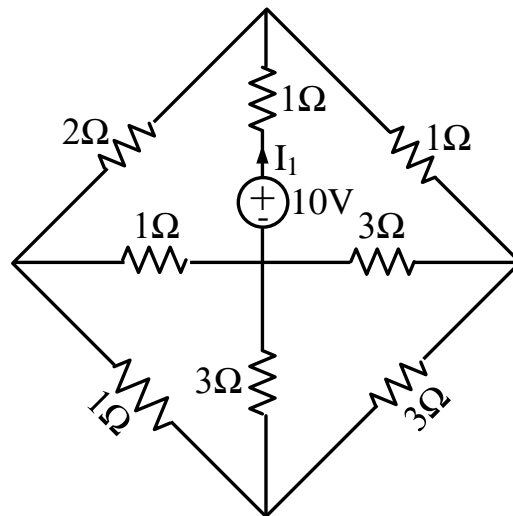Q11 Find current I_1 in the 1 ohm resistance as shown using Thevenin's theorem.



[Ans $V_{Th} = -10V$, $R_{Th} = 1.5\Omega$, and $I_1 = 4.0A$]

Q12 Find current I in the circuit.

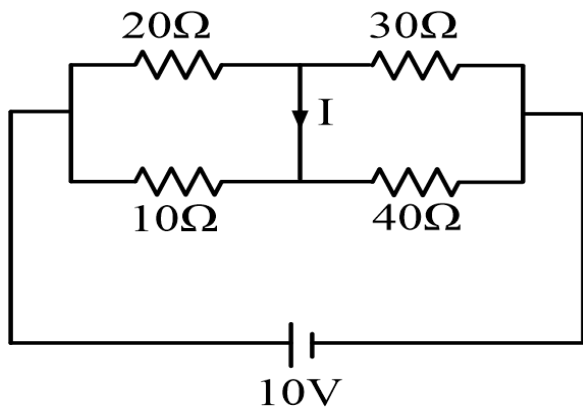

[Ans $I = -0.1A$]